

# Two Hardware Description Languages

## ■ Verilog

- developed in 1984 by Gateway Design Automation
- became an IEEE standard (1364) in 1995
- More popular in US

## ■ VHDL (VHSIC Hardware Description Language)

- Developed in 1981 by the Department of Defense
- Became an IEEE standard (1076) in 1987
- More popular in Europe

## ■ In this course we will use Verilog


# Defining a module

- A module is the main building block in Verilog
- We first need to declare:
  - Name of the module
  - Types of its connections (input, output)
  - Names of its connections


 
# Defining a module

```
module example (a, b, c, y);  
    input a;  
    input b;  
    input c;  
    output y;  
  
    // here comes the circuit description  
  
endmodule
```



# A question of style

*The following two codes are identical*

```
module test ( a, b, y );  
    input a;  
    input b;  
    output y;  
  
endmodule
```

```
module test ( input a,  
              input b,  
              output y );  
  
endmodule
```

# What if we have busses?

- You can also define multi-bit busses.

- [ range\_start : range\_end ]

- Example:

```
input  [31:0] a;    // a[31], a[30] .. a[0]
output [15:8] b1;   // b1[15], b1[14] .. b1[8]
output [7:0]  b2;   // b2[7], b2[6] .. b1[0]
input          clk; // single signal
```

# Basic Syntax

- Verilog is case sensitive:
  - `SomeName` and `somename` are not the same!
- Names cannot start with numbers:
  - `2good` is not a valid name
- Whitespace is ignored

```
// Single line comments start with a //  
  
/* Multiline comments  
   are defined like this */
```

# Good Practices

- Develop/use a consistent naming style
- Use MSB to LSB ordering for busses (little-endian)
  - Try using “a[31:0]” and not “a[0:31]”
- Define one module per file
  - Makes managing your design hierarchy easier
- Use a file name that equals module name
  - i.e. module TryThis is defined in a file called TryThis.v

# There are Two Main Styles of HDL

## ■ Structural

- Describe how modules are interconnected
- Each module contains other modules (instances)
- ... and interconnections between these modules
- Describes a hierarchy


## ■ Behavioral

- The module body contains functional description of the circuit
- Contains logical and mathematical operators

## ■ Practical circuits would use a combination of both



# Structural HDL: Instantiating a Module

 


# Structural HDL Example

## Module Definitions

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
// description of small
```


```
endmodule
```

# Structural HDL Example

## Module Definitions

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
// description of small
```


```
endmodule
```

# Structural HDL Example

## Wire definitions

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
// description of small
```

```
endmodule
```


# Structural HDL Example

## *Instantiate first module*

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
  // instantiate small once  
  small i_first ( .A(A),  
                  .B(SEL),  
                  .Y(n1) );
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
  // description of small
```

```
endmodule
```

# Structural HDL Example


## *Instantiate second module*

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
  // instantiate small once  
  small i_first ( .A(A),  
                  .B(SEL),  
                  .Y(n1) );
```

```
  // instantiate small second time  
  small i2 ( .A(n1),  
             .B(C),  
             .Y(Y) );
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
  // description of small
```

```
endmodule
```

# Structural HDL Example

## Short Instantiation


```
module top (A, SEL, C, Y);
  input A, SEL, C;
  output Y;
  wire n1;

  // alternative
  small i_first ( A, SEL, n1 );

  /* Shorter instantiation,
     pin order very important */

  // any pin order, safer choice
  small i2 ( .B(C),
             .Y(Y),
             .A(n1) );

endmodule
```

 

```
module small (A, B, Y);
  input A;
  input B;
  output Y;

  // description of small

endmodule
```

# What Happens with HDL code?

## ■ Automatic Synthesis

- Modern tools are able to map a behavioral HDL code into gate-level schematics
- They can perform many optimizations
- ... however they can not guarantee that a solution is optimal
- Most common way of Digital Design these days

## ■ Simulation

- Allows the behavior of the circuit to be verified without actually manufacturing the circuit
- Simulators can work on behavioral or gate-level schematics



# Behavioral HDL: Defining Functionality

```
module example (a, b, c, y);  
    input a;  
    input b;  
    input c;  
    output y;  
  
    // here comes the circuit description  
    assign y = ~a & ~b & ~c |  
               a & ~b & ~c |  
               a & ~b & c;  
  
endmodule
```